

Computer System Architecture

Processor Part I


Chalermek Intanagonwiwat

Slides courtesy of John Hennessy and David Patterson

The Big Picture: The Performance Perspective

- Performance of a machine is determined by:

 - Instruction count
- Clock cycle time
- Clock cycles per instruction



The Big Picture (cont.)


- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Today:
 - Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

How to Design a Processor: step-by-step

 
1. Analyze instruction set => datapath requirements
 - the meaning of each instruction is given by the *Register Transfer Language (RTL)*
 - datapath must include storage element for ISA registers
 - possibly more
 - datapath must support each register transfer

Step 1a: The MIPS-lite Subset (cont.)

- LOAD and STORE Word
 - lw rt, rs, imm16
 - sw rt, rs, imm16



- BRANCH:
 - beq rs, rt, imm16

 

Logical Register Transfers

- RTL gives the meaning of the instructions
- All start by fetching the instruction

Logical Register Transfers (cont.)

op | rs | rt | rd | shamt | funct = MEM[PC]
 op | rs | rt | Imm16 = MEM[PC]

inst	Register Transfers
ADDU	R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU	R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORI	R[rt] ← R[rs] zero_ext(Imm16); PC ← PC + 4
LOAD	R[rt] ← MEM[R[rs] + sign_ext(Imm16)]; PC ← PC + 4
STORE	MEM[R[rs] + sign_ext(Imm16)] ← R[rt]; PC ← PC + 4
BEQ	if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) 00 else PC ← PC + 4

Step 1: Requirements of the Instruction Set

- Memory
 - instruction & data
- Registers (32 x 32)
 - read RS
 - read RT
 - Write RT or RD
- PC

Step 1: Requirements of the Instruction Set (cont.)


- Extender
- Add and Sub register or extended immediate
- Add 4 or extended immediate to PC

Step 2: Components of the Datapath


- Combinational Elements
- Storage Elements
 - Clocking methodology

Combinational Logic Elements


- Adder

 

- MUX

 


- ALU

 

Storage Element: Register

- Similar to the D Flip Flop except

 - N-bit input and output
- Write Enable input




- Write Enable:

- negated (0): Data Out will not change
- asserted (1): Data Out will become Data In

Register File

 - Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW



Register File (cont.)


- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1

Register File (cont.)

- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after "access time."


Register File (cont.)

- Built using D flip-flops

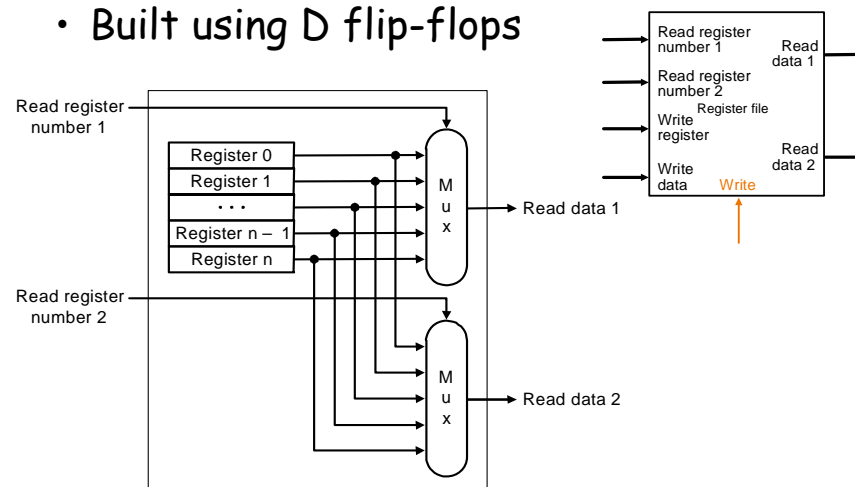


Register File (cont.)

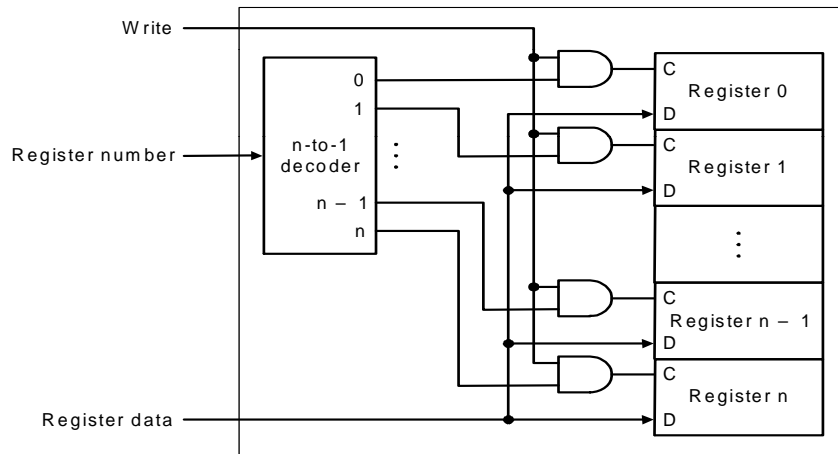- Note: we still use the real clock to determine when to write



Storage Element: Idealized Memory

 - Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out



Storage Element: Idealized Memory (cont.)

- Memory word is selected by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus

Storage Element: Idealized Memory (cont.)

- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after "access time."


Step 3

- Register Transfer Requirements
-> Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation

3a: Overview of the Instruction Fetch Unit

- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$


 
3a: Overview of the Instruction Fetch Unit (cont.)




3b: Add & Subtract

- $R[\text{rd}] \leftarrow R[\text{rs}] \text{ op } R[\text{rt}]$
Example: `addU rd, rs, rt`
 - Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction

3b: Add & Subtract (cont.)

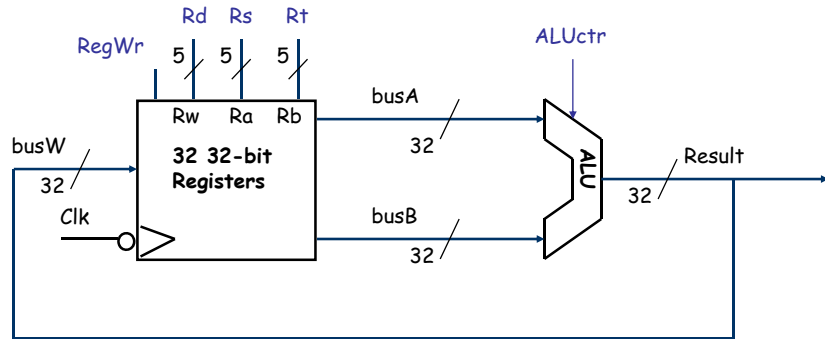
 


Register-Register Timing

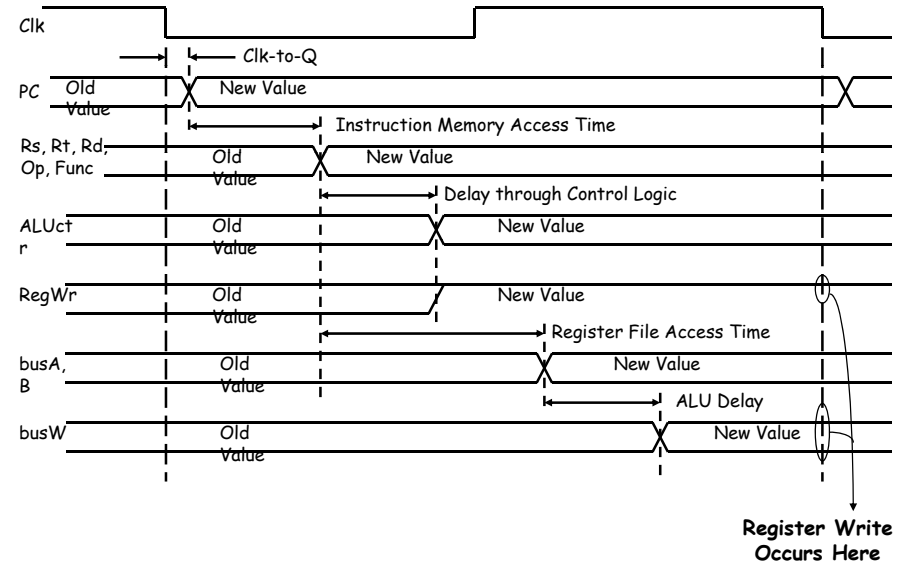


3c: Logical Operations with Immediate
  
$$R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$$




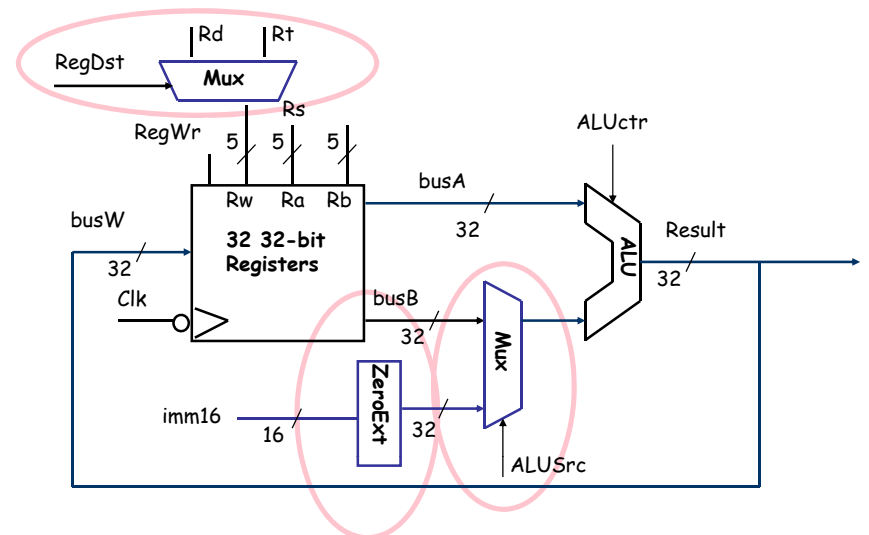3c: Logical Operations with Immediate (cont.)




3d: Load Operations

 - $R[rt] \leftarrow Mem[R[rs] + SignExt[imm16]]$
 Example: lw rt, rs, imm16




3d: Load Operations (cont.)

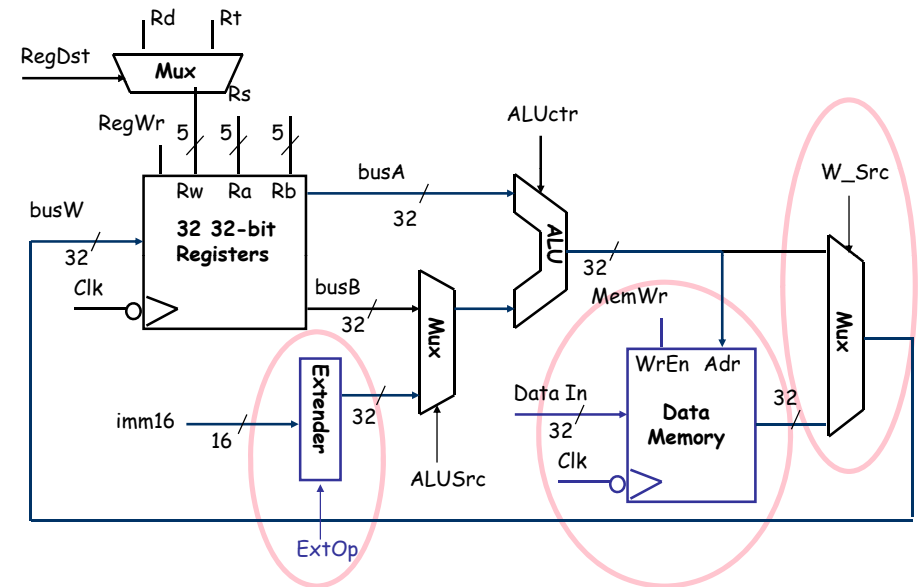


3e: Store Operations

 
- $Mem[R[rs] + SignExt[imm16]] \leftarrow R[rt]$
 Example: sw rt, rs, imm16



3e: Store Operations (cont.)

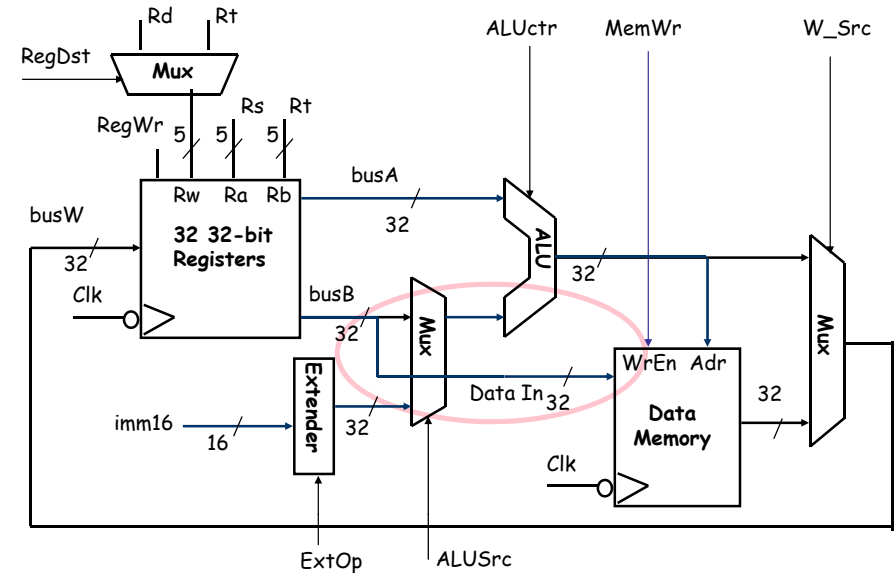


3f: The Branch Instruction

 


- `beq rs, rt, imm16`
 - `mem[PC]` Fetch the instruction from memory
 - `Equal <- R[rs] == R[rt]` Calculate the branch condition
 - if (`COND eq 0`) Calculate the next instruction's address
 - $PC \leftarrow PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$
 - else
 - $PC \leftarrow PC + 4$

Datapath for Branch Operations

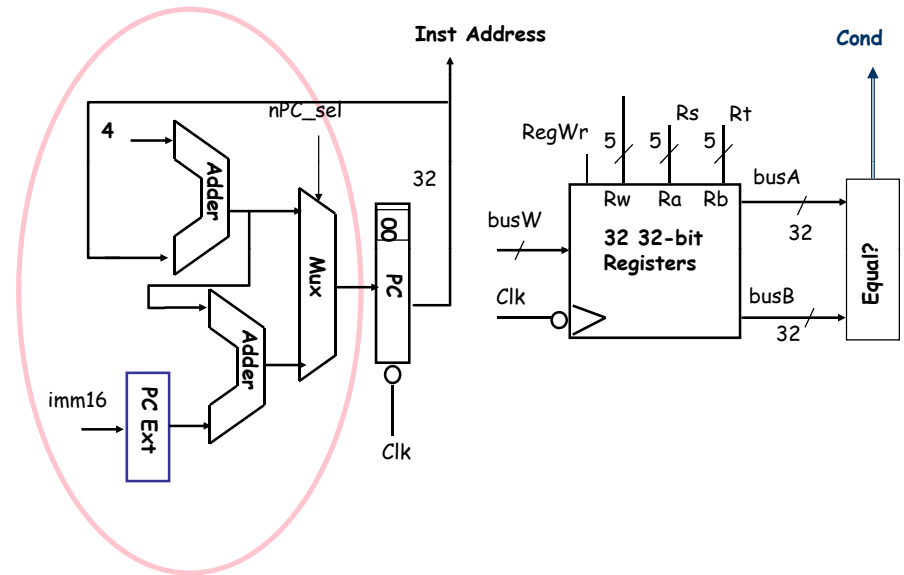


A Single Cycle Datapath

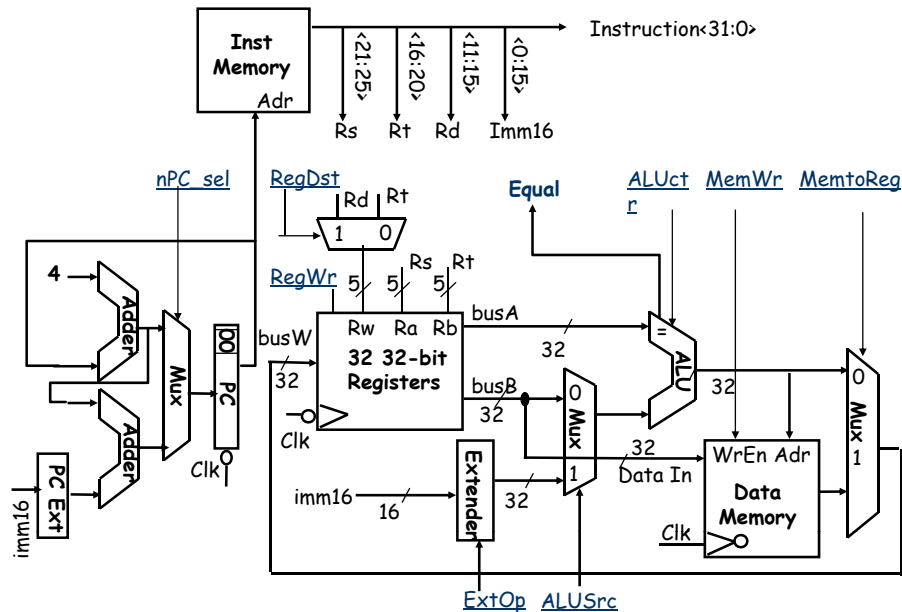


An Abstract View of the Critical Path

- Register file and ideal memory:
 - The CLK input is a factor ONLY during write operation
 - During read operation, behave as combinational logic:
 - Address valid => Output valid after "access time."

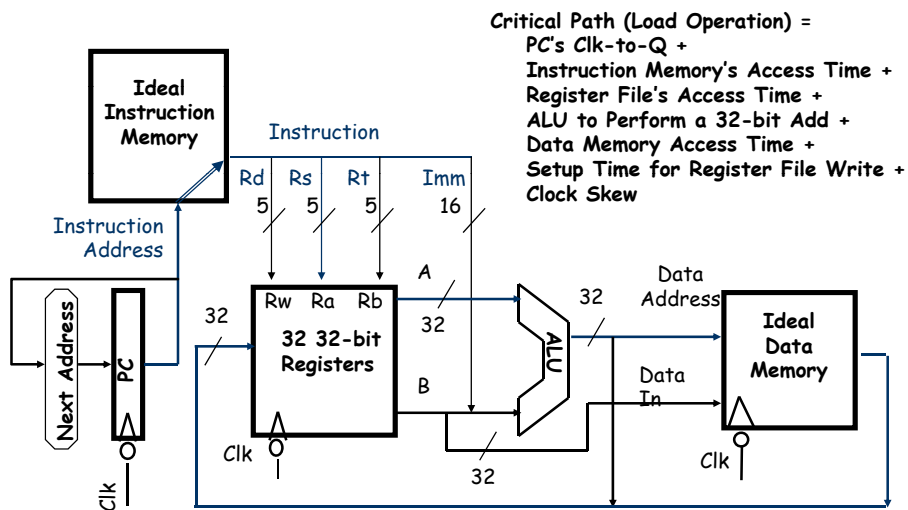
An Abstract View of the Critical Path (cont.)



Step 4: Given Datapath: RTL -> Control

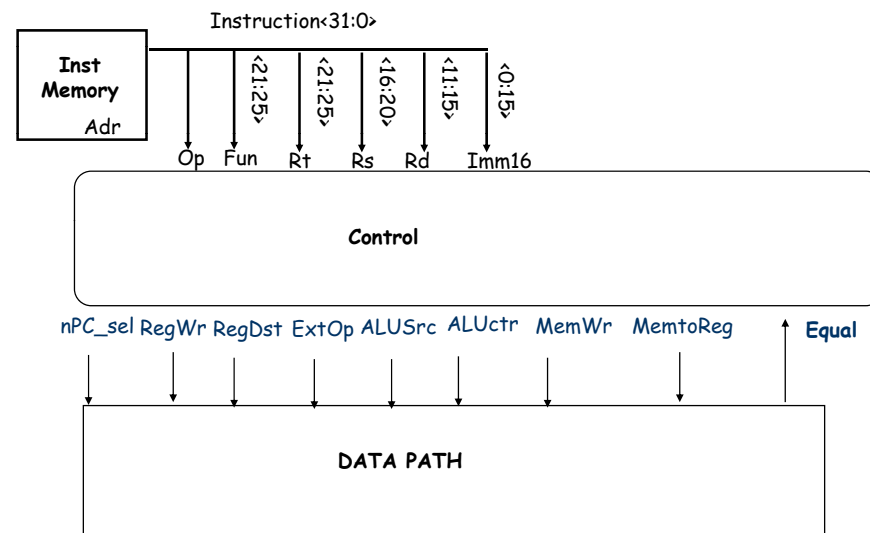


Meaning of the Control Signals

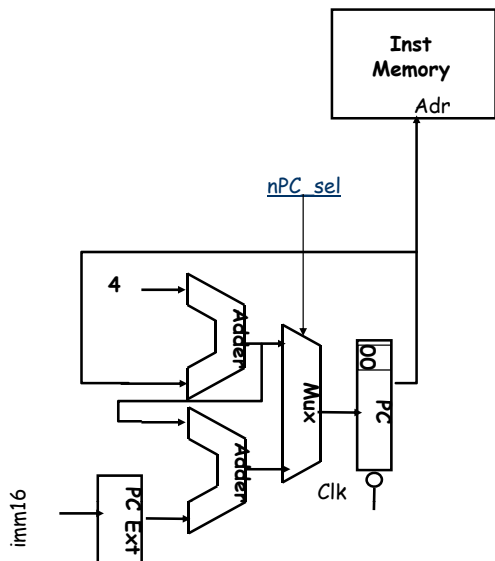

Meaning of the Control Signals (cont.)

- Rs, Rt, Rd and Imed16 hardwired into datapath
- nPC_sel:
 - 0 => $PC \leftarrow PC + 4;$
 - 1 => $PC \leftarrow PC + 4 + \text{SignExt}(\text{Im16}) \parallel 00$

Meaning of the Control Signals (cont.)

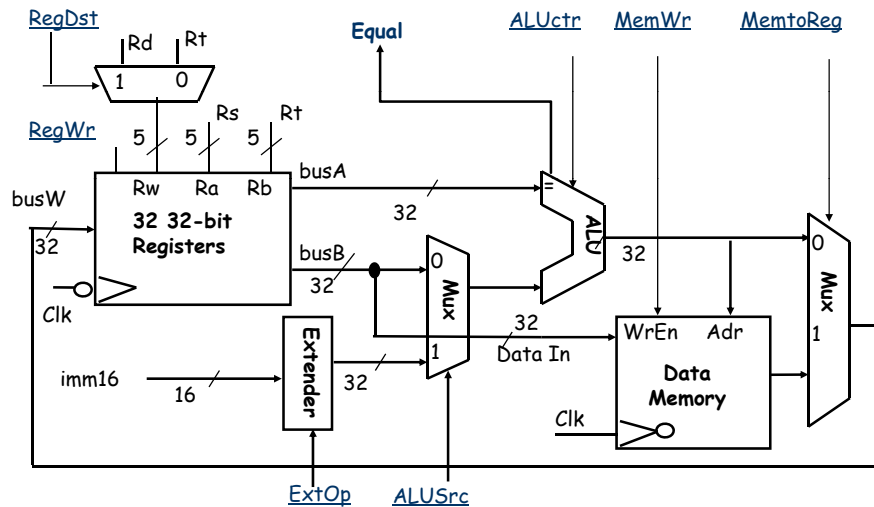

Meaning of the Control Signals (cont.)

- ExtOp: "zero", "sign"
- ALUsrc: 0 => regB; 1 => immed
- ALUctr: "add", "sub", "or"
- MemWr: write memory
- MemtoReg: 1 => Mem
- RegDst: 0 => "rt"; 1 => "rd"
- RegWr: write dest register

Control Signals (cont.)

inst Register Transfer

ADD R[rd] ← R[rs] + R[rt]; PC ← PC + 4
 ALUsrc = RegB, ALUctr = "add", RegDst = rd,
 RegWr, nPC_sel = "+4"

SUB R[rd] ← R[rs] - R[rt]; PC ← PC + 4
 ALUsrc = RegB, ALUctr = "sub", RegDst = rd,
 RegWr, nPC_sel = "+4"

ORI R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
 ALUsrc = Im, Extop = "Z", ALUctr = "or",
 RegDst = rt, RegWr, nPC_sel = "+4"

Control Signals (cont.)

LOAD R[rt] ← MEM[R[rs] + sign_ext(Imm16)];
 PC ← PC + 4

ALUsrc = Im, Extop = "Sn", ALUctr = "add",
 MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"

STORE MEM[R[rs] + sign_ext(Imm16)] ← R[rs];
 PC ← PC + 4

ALUsrc = Im, Extop = "Sn", ALUctr = "add",
 MemWr, nPC_sel = "+4"

BEQ if (R[rs] == R[rt]) then
 PC ← PC + sign_ext(Imm16) || 00 else PC ← PC + 4
 nPC_sel = EQUAL, ALUctr = "sub"


Step 5: Logic for each control signal

- $nPC_sel \leftarrow \text{if } (OP == BEQ) \text{ then EQUAL else } 0$
- $ALUsrc \leftarrow \text{if } (OP == R\text{-TYPE}) \text{ then "regB" else "immed"}$
- $ALUctr \leftarrow \text{if } (OP == R\text{-TYPE}) \text{ then "func" elseif } (OP == ORI) \text{ then "OR" elseif } (OP == BEQ) \text{ then "sub" else "add"}$


Step 5: Logic for each control signal (cont.)

- $ExtOp \leftarrow \text{if } (OP == ORI) \text{ then "zero" else "sign"}$
- $MemWr \leftarrow (OP == Store)$
- $MemtoReg \leftarrow (OP == Load)$
- $RegWr: \leftarrow \text{if } ((OP == Store) \parallel (OP == BEQ)) \text{ then } 0 \text{ else } 1$
- $RegDst: \leftarrow \text{if } ((OP == Load) \parallel (OP == ORI)) \text{ then } 0 \text{ else } 1$

Example: Load Instruction

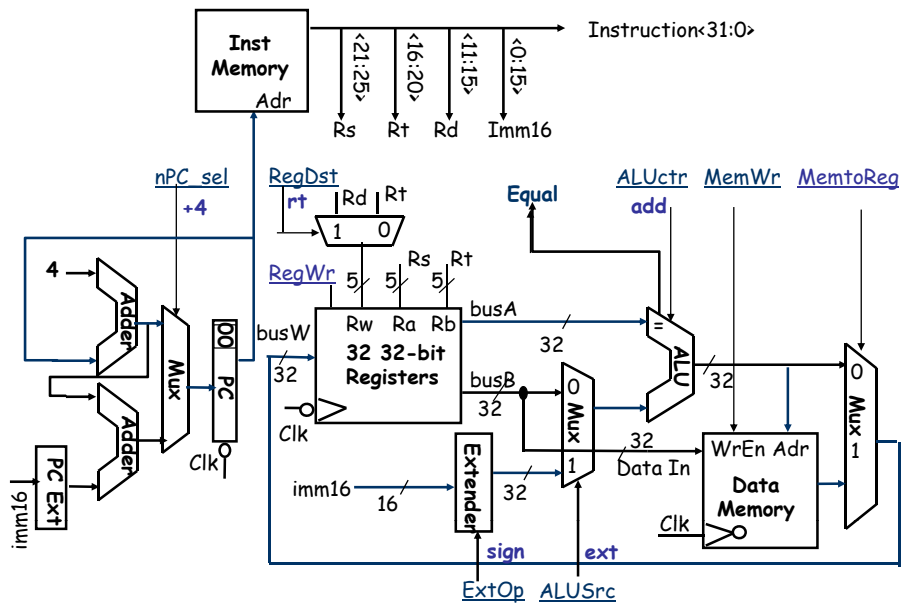

An Abstract View of the Implementation

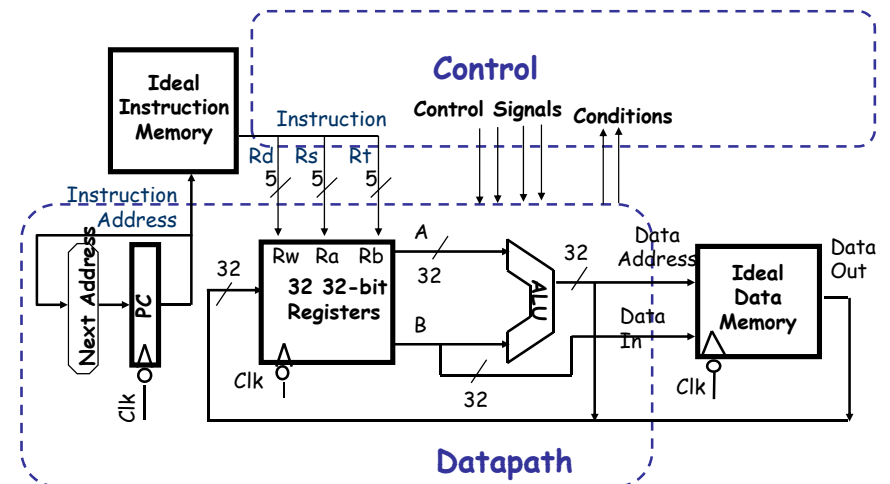

- Logical vs. Physical Structure

Summary

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic

Summary (cont.)

- MIPS makes it easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- Single cycle datapath => $CPI=1$, $CCT \Rightarrow$ long
- Next time: implementing control