

BASIC LOGIC DESIGN

LOGICAL OPERATIONS


- Logical operations (Boolean algebra)
- named after George Boole, a famous mathematician
- AND, OR, NOT, XOR, NAND, NOR

LOGICAL OPERATIONS

NOT Gate

- operates on one bit
- logical reverse (usually denoted by "!" or "~")
- $!0 = \sim 0 = 1$
- $!1 = \sim 1 = 0$

NOT

 


INPUT	OUTPUT
A	
0	1
1	0

LOGICAL OPERATIONS

AND Gate

 - operates on two bits
- logical and (usually denoted by "&" or "."): both have to be true




INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

LOGICAL OPERATIONS

OR Gate

- operates on two bits
- logical or (usually denoted by " $|$ " or " $+$ "): at least one has to be true

 

INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

LOGICAL OPERATIONS

XOR Gate

- operates on two bits
- logical exclusive or (usually denoted by " \oplus "): only one is true

XOR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

LOGICAL OPERATIONS

NAND and NOR

- NAND = NOT AND
- NOR = NOT OR

- $A \text{ NAND } B = \neg(A \cdot B)$
- $A \text{ NOR } B = \neg(A + B)$

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

LOGICAL OPERATIONS

NAND and NOR are very convenient

- You can build any other gate out of NANDs and NORs
- So, any circuit can be built out of just NANDs or NORs

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

LOGICAL OPERATIONS

NOT out of NAND

$$\neg(A) = A \text{ NAND } A$$

AND out of NAND

$$A \text{ AND } B = (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$$

OR out of NAND

$$A \text{ OR } B = (A \text{ NAND } A) \text{ NAND } (B \text{ NAND } B)$$

DE MORGAN'S LAWS

$$\overline{(A \cdot B)} = \bar{A} + \bar{B}$$

$$\overline{(A + B)} = \bar{A} \cdot \bar{B}$$

DIGITAL CIRCUITS

With basic gates and logical operations, you can build any logical functions or arithmetic functions.

For example, if you want to choose something based on a condition

**i.e. if $S = 0$, choose A,
if $S = 1$, choose B.**

SIMPLE DIGITAL CIRCUIT

If $S = 0$, choose A,
if $S = 1$, choose B.

A	B	S	Output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

SIMPLE DIGITAL CIRCUIT

If $S = 0$, choose A,
if $S = 1$, choose B.

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

SIMPLE DIGITAL CIRCUIT

If $S = 0$, choose A,
if $S = 1$, choose B.

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

SIMPLE DIGITAL CIRCUIT

If $S = 0$, choose A,
if $S = 1$, choose B.

A	B	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$Output = \bar{A} \cdot B \cdot S + A \cdot \bar{B} \cdot \bar{S} + A \cdot B \cdot \bar{S} + A \cdot B \cdot S$$

Can you simplify this?

SIMPLE DIGITAL CIRCUIT

$$\text{Output} = \bar{A} \cdot B \cdot S + A \cdot \bar{B} \cdot \bar{S} + A \cdot B \cdot \bar{S} + A \cdot B \cdot S$$

If $S = 0$, choose A ,
if $S = 1$, choose B .

- Identity law: $A+0=A$ and $A \cdot 1=A$
- Zero and One laws: $A+1=1$ and $A \cdot 0=0$
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A+B=B+A$ and $A \cdot B=B \cdot A$
- Associative laws: $A+(B+C)=(A+B)+C$ and $A \cdot (B \cdot C)=(A \cdot B) \cdot C$
- Distributive laws: $A \cdot (B+C)=(A \cdot B)+(A \cdot C)$ and $A+(B \cdot C)=(A+B) \cdot (A+C)$

SIMPLE DIGITAL CIRCUIT

Can you simplify this?

$$\text{Output} = \bar{A} \cdot B \cdot S + A \cdot \bar{B} \cdot \bar{S} + A \cdot B \cdot \bar{S} + A \cdot B \cdot S$$

$$\text{Output} = S (\bar{A}B + AB) + \bar{S} (A\bar{B} + AB)$$

If $S = 0$, choose A ,
if $S = 1$, choose B .

$$\text{Output} = SB (\bar{A} + A) + \bar{S}A (\bar{B} + B)$$

$$\text{Output} = SB + \bar{S}A$$

- Identity law: $A+0=A$ and $A \cdot 1=A$
- Zero and One laws: $A+1=1$ and $A \cdot 0=0$
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A+B=B+A$ and $A \cdot B=B \cdot A$
- Associative laws: $A+(B+C)=(A+B)+C$ and $A \cdot (B \cdot C)=(A \cdot B) \cdot C$
- Distributive laws: $A \cdot (B+C)=(A \cdot B)+(A \cdot C)$ and $A+(B \cdot C)=(A+B) \cdot (A+C)$

Can you simplify this?

SIMPLE DIGITAL CIRCUIT

If $S = 0$, choose A ,
if $S = 1$, choose B .

Using K-MAP

		BS			
		00	01	11	10
A	0	0	0	1	0
	1	1	0	1	1

- Identity law: $A+0=\bar{A}$ and $A\cdot 1=A$
- Zero and One laws: $A+1=1$ and $A\cdot 0=0$
- Inverse laws: $A+\bar{A}=1$ and $A\cdot\bar{A}=0$
- Commutative laws: $A+B=B+A$ and $A\cdot B=B\cdot A$
- Associative laws: $A+(B+C)=(A+B)+C$ and $A\cdot(B\cdot C)=(A\cdot B)\cdot C$
- Distributive laws: $A\cdot(B+C)=(A\cdot B)+(A\cdot C)$ and $A+(B\cdot C)=(A+B)\cdot(A+C)$

MULTIPLEXOR 2:1

very common circuit where the name is
MUX (# of inputs) : (# of output)

 


FIGURE A.3.2 A two-input multiplexer on the left and its implementation with gates on the right.

BUILDING AN ADDER

- Let's do an arithmetic circuit
- An adder which adds two 1-bit together

A	B	R	Carry-out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

BUILDING AN ADDER

- 1-bit adder actually needs two outputs
- One for the output
- One for the carry-out

A	B	R	Carry-out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

BUILDING AN ADDER

- 1-bit adder actually needs two outputs
- One for the output
- One for the carry-out

A	B	R	Carry-out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Output functions

- $R = A \oplus B$
- $\text{Carry-out} = A.B$

BUILDING AN ADDER

- 1-bit adder actually needs two outputs
- One for the output
- One for the carry-out


A	B	R	Carry-out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Output functions

- $R = A \oplus B$
- $\text{Carry-out} = A.B$

BUILDING AN ADDER

- This circuit is called, “Half Adder”

 



A	B	R	Carry-out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Output functions

- $R = A \oplus B$
- $\text{Carry-out} = A.B$

BUILDING AN ADDER

  - To add more than two 1-bits together, the adder must add the carry from the other adder




BUILDING AN ADDER

- Full Adder has 3 inputs and 2 outputs.

Carry-in	A	B	R	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

BUILDING AN ADDER

 
- Full Adder has 3 inputs and 2 outputs.
- Can use 2 half-adders



Carry-in	A	B	R	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

BUILDING AN ADDER

- Full Adder has 3 inputs and 2 outputs.

 

Block diagram representation of the Full Adder

Carry-in	A	B	R	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

