



Verilog HDL: Tip & Trick Pitfalls, Fallacies, Good designs

Krerk Piromsopa, Ph.D
Department of Computer Engineering
Chulalongkorn University

Outline & Target

- Outline
 - Revisit basic knowledge of Verilog
 - Emphasis on Design Pitfall
- Goals
 - After this class, if you have a better idea of using Verilog as a language to describe your design, I have succeed.

Basic

- Four-Value Logic
 - 0, 1 , x (unknown), z (high impedance)
- number representation
 - 6'b10_011, 16'hx
 - 6'b_101111 WRONG

Basic

- Parameter is a constant, can only be integer
 - **parameter WIDTH = 32, depth = 1024;**
- Nets, Registers
- bitwise and logic
- comparison ==, === (only w===v)
- case, casex


Basic

- Concatenation
 - { cout, sum }
- Replication
 - {8{2'b01}};
-

Basic

- Variable Part-Select (Verilog 2001)
 - `sum[K+:3] --- {sum[K+2],sum[K+1],sum[K]}`
- Memories
 - **parameter** WIDTH = 32, depth = 1024
 - **reg** [WIDTH-1:0] cache [0:depth-1];
 - **reg** [WIDTH-1:0] cache [0: 2**WIDTH -1]; // (Verilog 2001)

Input/Output

 

Common Notation

Output before input

- | | |
|---|---|
| <ul style="list-style-type: none"> • Verilog 1995 <pre> module add (sum, c_out, a, b); output sum, c_out; input a,b; </pre> | <ul style="list-style-type: none"> • Verilog 2001 <pre> module add(output sum, c_out, input a,b); </pre> |
|---|---|

User-defined primitives (UDPs)

```
primitive latch(q_out,en, data);
output reg q_out;
input en, data;

table
// en data : state : q_out/next_state
1 1 : ? : 1;
1 0 : ? : 0;
0 ? : ? : -;
x 0 : 0 : -;
x 1 : 1 : -;

endtable

endprimitive
```

Assignment

- Continuous assignment
 - $a = b \& c;$
 - left-handed side must be net.
- Procedural assignment
 - in always
 - left-handed size must be reg.

Event

```
always @ (events) begin
```

```
end
```



Concurrent

- events are synchronization signals or all sensitivity list.
- posedge , negedge

Overriding Parameters

```
module adder (sum,
c_out,a,b);
parameter width=4;
output reg [width-1:0]
sum;
output reg c_out;
input [width-1:0] a,b;
always @(a,b) begin
    {c_out,sum} = a+b;
end
endmodule
```

```
module top();
....
// 8 bit adder
adder #(8) add8(....)
// 16 bit adder
adder #(16) add16 (...)
endmodule
```

For

```
input [7:0] A
output reg Valid;
output reg [2:0] Y;
integer i;
```

```
always @(A) begin
Valid=0;
Y=3'bX;
for(i=0;i<8;i=i+1)
    if (A(i)) begin
        Valid=1;
        Y=N;
    end
end
```

```
input [7:0] A
output reg Valid;
output reg [2:0] Y;
integer i;
always @(A) begin
    Valid=1;
    casex(A)
        8'b1XXX_XXXX : Y=7;
        8'b01XX_XXXX : Y=6;
        8'b001X_XXXX : Y=5;
        8'b0001_XXXX : Y=4;
        8'b0000_1XXX : Y=3;
        8'b0000_01XX : Y=2;
        8'b0000_001X : Y=1;
        8'b0000_0001 : Y=0;
        default: begin
            Valid=0;
            Y=3'bX;
        end
    endcase
end
endmodule
```

Pitfalls

Common Pitfall

- Verilog is not a programming language, but a HDL.
- Don't try to debug a design that doesn't work.
- Don't use Latches or Flip-Flops in combinational circuit.



Blocking vs. NonBlocking

```
module shiftReg1(out,d, clock);
output reg [3:0] out;
input d, clock;
always @(posedge clock) begin
    out[0]=d;
    out[1]=out[0];
    out[2]=out[1];
    out[3]=out[2];
end
endmodule
```

```
module shiftReg2(out,d, clock);
output reg [3:0] out;
input d, clock;
```

```
always @(posedge clock) begin
    out[3]=out[2];
    out[2]=out[1];
    out[1]=out[0];
    out[0]=d;
end
```

```
endmodule
```

 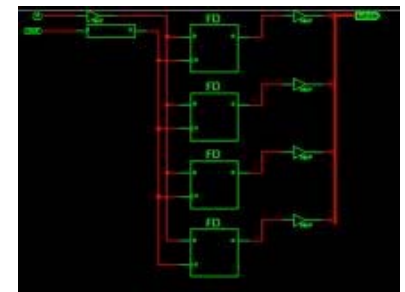

Blocking vs. NonBlocking

```
module shiftReg3(out,d, clock);
output reg [3:0] out;
input d, clock;
```

```
always @(posedge clock) begin
    out[0]<=d;
    out[1]<=out[0];
    out[2]<=out[1];
    out[3]<=out[2];
end
```

```
endmodule
```

```
module shiftReg4(out,d, clock);
output reg [3:0] out;
input d, clock;
```


```
always @(posedge clock) begin
    out[3]<=out[2];
    out[2]<=out[1];
    out[1]<=out[0];
    out[0]<=d;
end
```

```
endmodule
```

FSM Behaviors

- Finite State Machine (FSM)
 - state register
 - combinational logic

Good vs. Bad

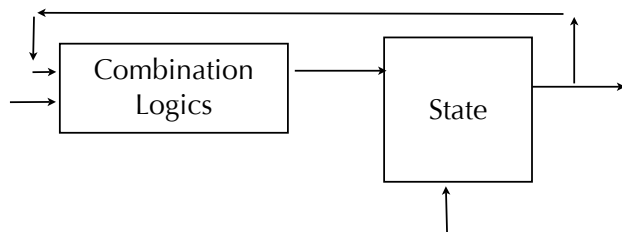

```
always @(posedge clock) begin
    ps=ns;
end

always @([input], ps) begin
end
```


Good

```
always @(posedge clock) begin
    case ...
        ....
        ....
        ...
    end
```

Bad

Output Assignment

 - FSM outputs should be combinational functions of Current State (Moore) and/or Input (Mealy)
- No assignment assumes output is a memory. Thus it is not FSM.



```
case State
  S: begin
    A<=0;
    B<=1;
  end
  T: begin
    C<=1;
  end
endcase
```

```
case State
  S: begin
    A<=0;
    B<=1;
    C<=0;
  end
  T: begin
    A<=0;
    B<=0;
    C<=1;
  end
endcase
```

```
A<=0;
B<=0;
C<=0;
case State
  S: begin
    B<=1;
  end
  T: begin
    C<=1;
  end
endcase
```

Ambiguous

- Unknown State
 - Always have reset signal
 - Default State
- Unknown Logic
 - Case with default
 - If with else

Implicit Declaration

```
output [3:0] X;  
  
input [3:0] a,b;  
  
assign X=y;  
  
always @(a,b) begin  
  
y=a&b;  
  
end
```

Guideline

- Think as a circuit designer, not a programmer

References

- on-line resources:
- http://www.sutherland-hdl.com/on-line_ref_guide/vlog_ref_top.html
- <http://www.engineering.usu.edu/classes/ece/2530/appendb.pdf>
- <http://www.asic-world.com/verilog/vqref.html>
- <http://oldeee.see.ed.ac.uk/~gerard/Teach/Verilog/>
- Google is your friend.