

Computer System Architecture

Processor Part I


Chalermek Intanagonwiwat

Slides courtesy of John Hennessy and David Patterson

The Big Picture: The Performance Perspective

- Performance of a machine is determined by:

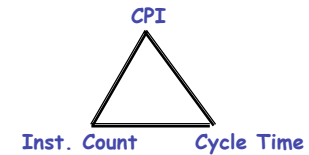- Instruction count
- Clock cycle time
- Clock cycles per instruction



The Big Picture (cont.)

- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Today:
 - Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

How to Design a Processor: step-by-step


1. Analyze instruction set => datapath requirements
 - the meaning of each instruction is given by the *Register Transfer Language (RTL)*
 - datapath must include storage element for ISA registers
 - possibly more
 - datapath must support each register transfer

How to Design a Processor (cont.)

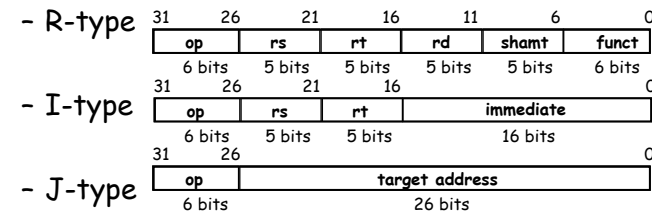2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic

The MIPS Instruction Formats

- All MIPS instructions are 32 bits long.
The three instruction formats:




The MIPS Instruction Formats (cont.)


- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination register specifiers
 - shamt: shift amount
 - funct: selects the variant of the operation in the "op" field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

Step 1a: The MIPS-lite Subset

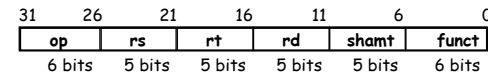- ADD and SUB
 - addU rd, rs, rt
 - subU rd, rs, rt




- OR Immediate:
 - ori rt, rs, imm16

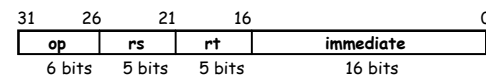

Step 1a: The MIPS-lite Subset (cont.)


- LOAD and STORE Word

- lw rt, rs, imm16
- sw rt, rs, imm16

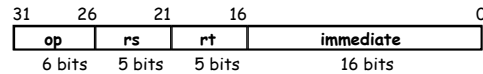

- BRANCH:

- beq rs, rt, imm16

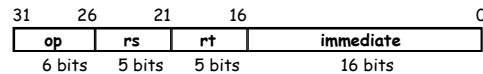

Logical Register Transfers

- RTL gives the meaning of the instructions
- All start by fetching the instruction

Logical Register Transfers (cont.)

op | rs | rt | rd | shamt | funct = MEM[PC]
 op | rs | rt | Imm16 = MEM[PC]

inst Register Transfers

ADDU R[rd] <- R[rs] + R[rt]; PC <- PC + 4
 SUBU R[rd] <- R[rs] - R[rt]; PC <- PC + 4
 ORI R[rt] <- R[rs] | zero_ext(Imm16); PC <- PC + 4
 LOAD R[rt] <- MEM[R[rs] + sign_ext(Imm16)]; PC <- PC + 4
 STORE MEM[R[rs] + sign_ext(Imm16)] <- R[rt]; PC <- PC + 4
 BEQ if (R[rs] == R[rt]) then
 PC <- PC + sign_ext(Imm16) || 00
 else PC <- PC + 4

Step 1: Requirements of the Instruction Set

- Memory
 - instruction & data
- Registers (32 x 32)
 - read RS
 - read RT
 - Write RT or RD
- PC

Step 1: Requirements of the Instruction Set (cont.)


- Extender
- Add and Sub register or extended immediate
- Add 4 or extended immediate to PC

Step 2: Components of the Datapath


- Combinational Elements
- Storage Elements
 - Clocking methodology

Combinational Logic Elements


- Adder

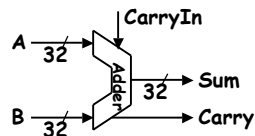

- MUX

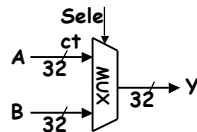


- ALU

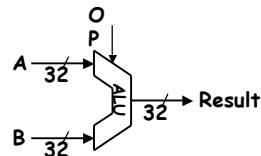

Storage Element: Register

- Similar to the D Flip Flop except

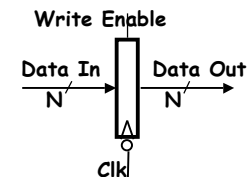- N-bit input and output
- Write Enable input




- Write Enable:

- negated (0): Data Out will not change
- asserted (1): Data Out will become Data In

Register File

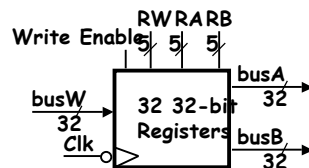- Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW



Register File (cont.)


- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1

Register File (cont.)

- Clock input (CLK)
 - The CLK input is a factor **ONLY** during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after "access time."


Register File (cont.)

- Built using D flip-flops

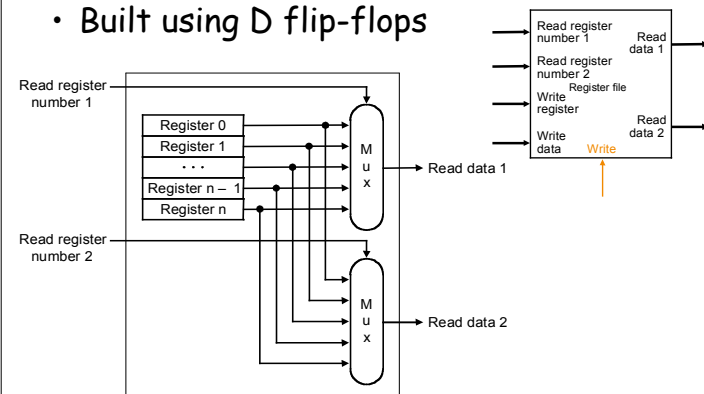


Register File (cont.)

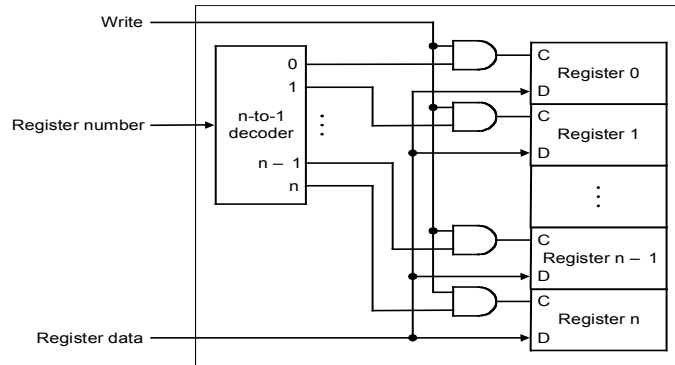- Note: we still use the real clock to determine when to write



Storage Element: Idealized Memory

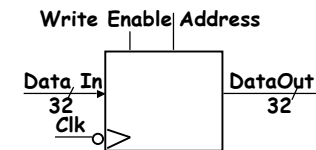- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out



Storage Element: Idealized Memory (cont.)

- Memory word is selected by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus

Storage Element: Idealized Memory (cont.)

- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after "access time."


Step 3

- Register Transfer Requirements
→ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation

3a: Overview of the Instruction Fetch Unit

- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$

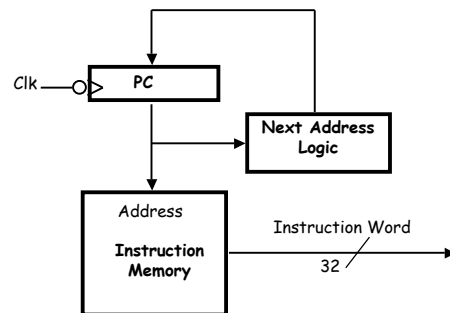
3a: Overview of the Instruction Fetch Unit (cont.)




3b: Add & Subtract

- $R[\text{rd}] \leftarrow R[\text{rs}] \text{ op } R[\text{rt}]$
Example: `addU rd, rs, rt`
 - Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction

3b: Add & Subtract (cont.)

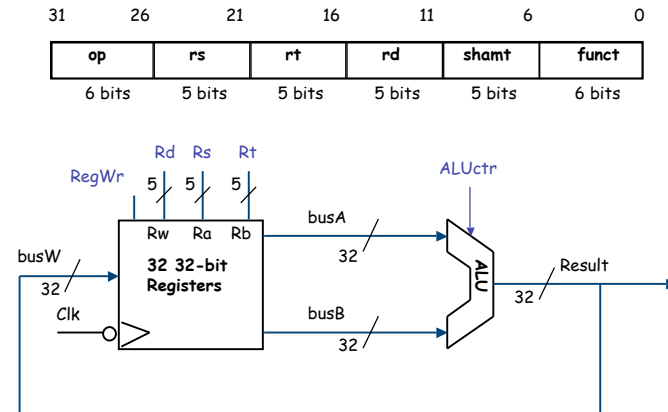


Register-Register Timing

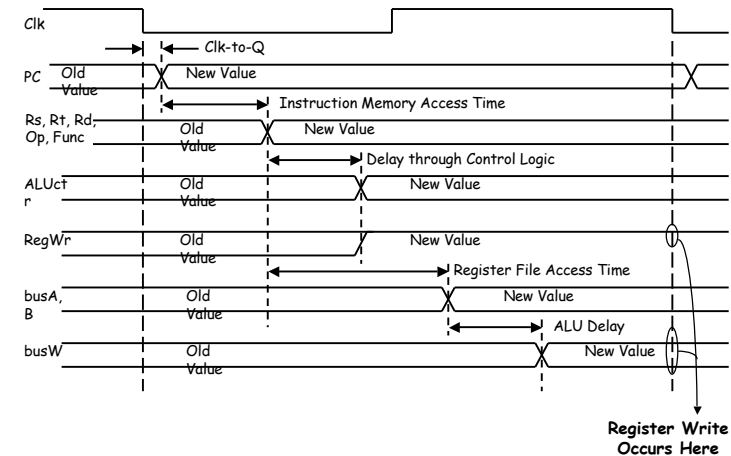


3c: Logical Operations with Immediate

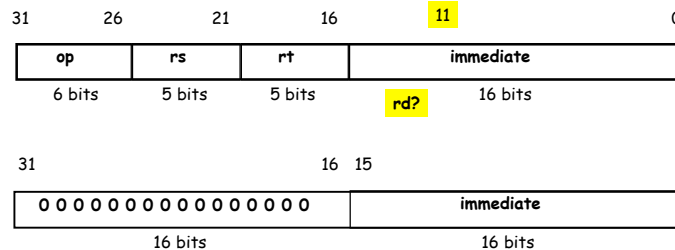• $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$




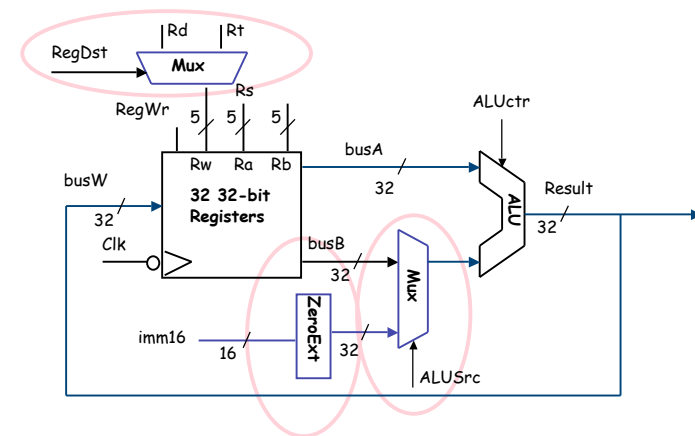3c: Logical Operations with Immediate (cont.)




3d: Load Operations

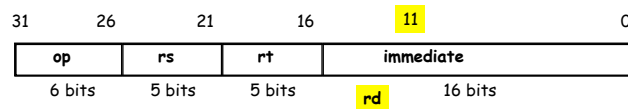- $R[r_t] \leftarrow \text{Mem}[R[r_s] + \text{SignExt}[\text{imm16}]]$
Example: lw rt, rs, imm16




3d: Load Operations (cont.)

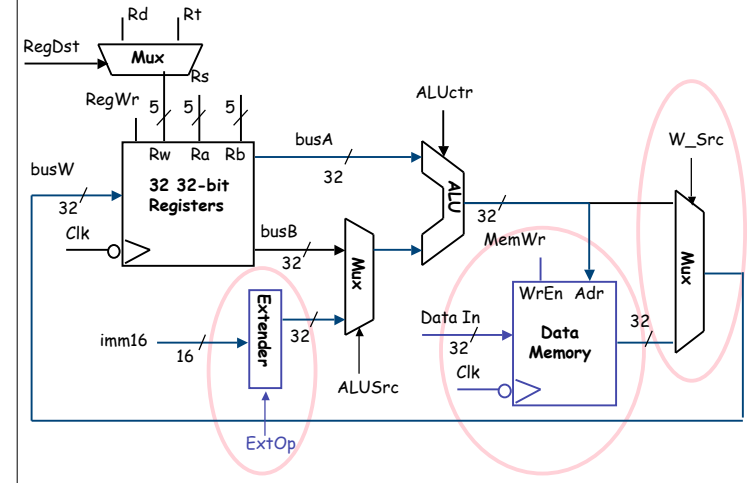


3e: Store Operations

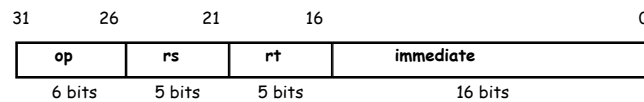
- $\text{Mem}[R[r_s] + \text{SignExt}[\text{imm16}]] \leftarrow R[r_t]$
Example: sw rt, rs, imm16



3e: Store Operations (cont.)

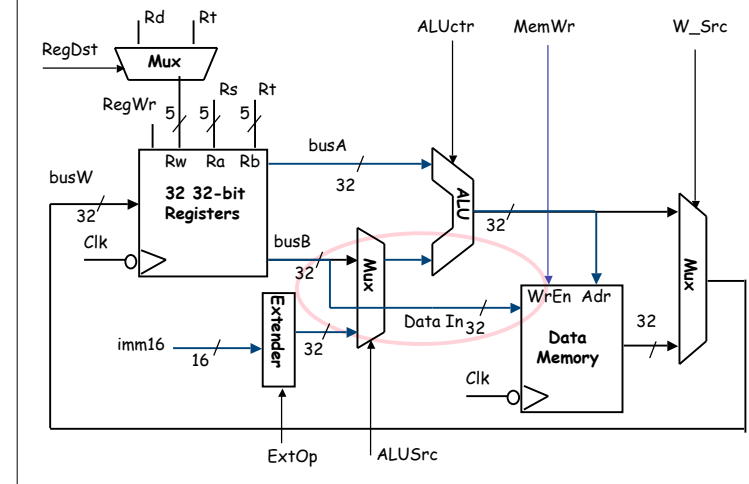


3f: The Branch Instruction

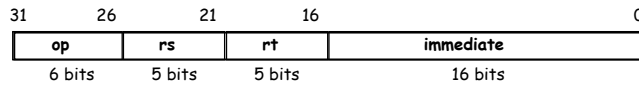


- beq rs, rt, imm16
 - mem[PC] Fetch the instruction from memory
 - Equal <- R[rs] == R[rt] Calculate the branch condition
 - if (COND eq 0) Calculate the next instruction's address
 - PC <- PC + 4 + (SignExt(imm16) x 4)
 - else
 - PC <- PC + 4

Datpath for Branch Operations

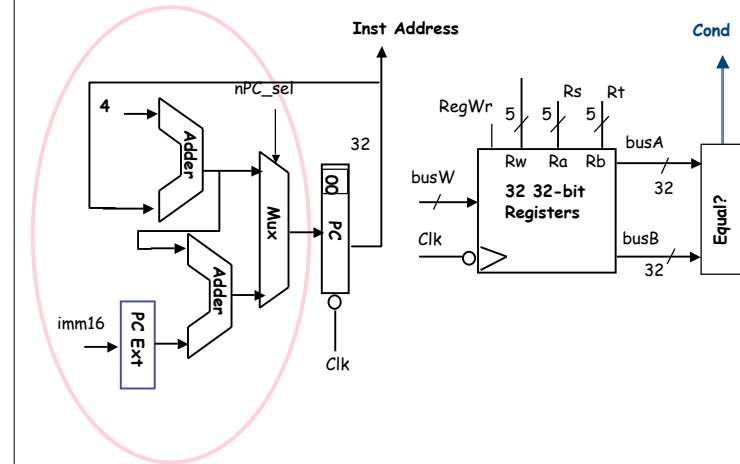


A Single Cycle Datapath

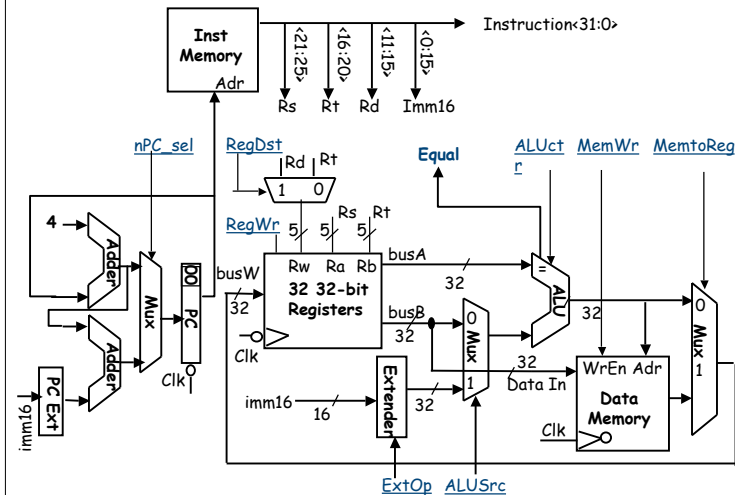


An Abstract View of the Critical Path

- Register file and ideal memory:
 - The CLK input is a factor ONLY during write operation
 - During read operation, behave as combinational logic:
 - Address valid => Output valid after "access time."

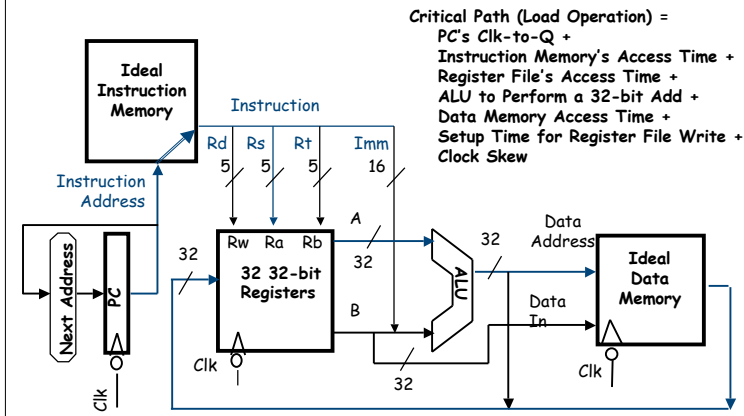
An Abstract View of the Critical Path (cont.)



Step 4: Given Datapath: RTL -> Control

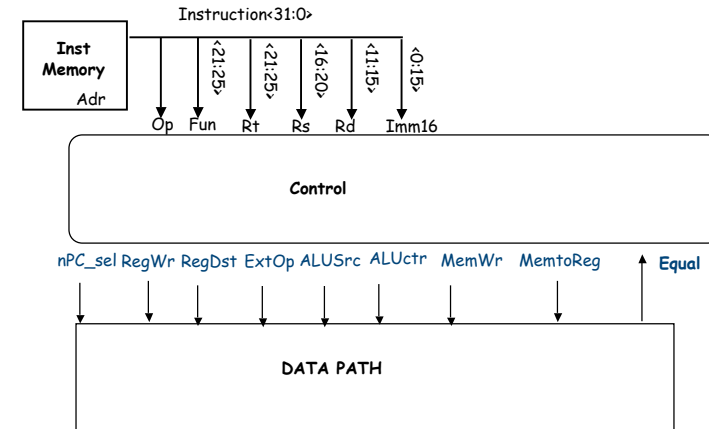


Meaning of the Control Signals

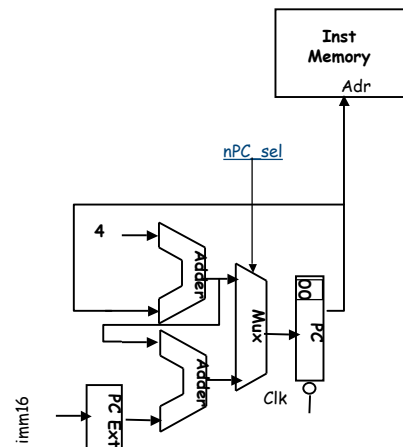

Meaning of the Control Signals (cont.)

- Rs, Rt, Rd and Imed16 hardwired into datapath
- nPC_sel:
 $0 \Rightarrow PC \leftarrow PC + 4;$
 $1 \Rightarrow PC \leftarrow PC + 4 + \text{SignExt}(\text{Im16}) \parallel 00$

Meaning of the Control Signals (cont.)

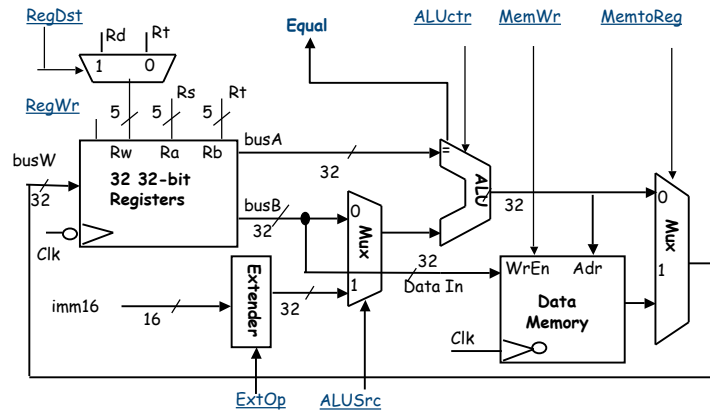

Meaning of the Control Signals (cont.)

- ExtOp: "zero", "sign"
- ALUSrc: 0 => regB; 1 => immed
- ALUctr: "add", "sub", "or"
- MemWr: write memory
- MemtoReg: 1 => Mem
- RegDst: 0 => "rt"; 1 => "rd"
- RegWr: write dest register

Control Signals (cont.)

inst Register Transfer

```

ADD  R[rd] <- R[rs] + R[rt];      PC <- PC + 4
      ALUSrc = RegB, ALUctr = "add", RegDst = rd,
      RegWr, nPC_sel = "+4"
SUB  R[rd] <- R[rs] - R[rt];      PC <- PC + 4
      ALUSrc = RegB, ALUctr = "sub", RegDst = rd,
      RegWr, nPC_sel = "+4"
ORi  R[rt] <- R[rs] + zero_ext(Imm16);  PC <- PC + 4
      ALUSrc = Im, Extop = "Z", ALUctr = "or",
      RegDst = rt, RegWr, nPC_sel = "+4"
    
```

Control Signals (cont.)

```

LOAD  R[rt] <- MEM[ R[rs] + sign_ext(Imm16)];
      PC <- PC + 4
      ALUSrc = Im, Extop = "Sn", ALUctr = "add",
      MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"
STORE  MEM[ R[rs] + sign_ext(Imm16)] <- R[rs];
      PC <- PC + 4
      ALUSrc = Im, Extop = "Sn", ALUctr = "add",
      MemWr, nPC_sel = "+4"
BEQ    if ( R[rs] == R[rt] ) then
      PC <- PC + sign_ext(Imm16)] || 00 else PC <- PC + 4
      nPC_sel = EQUAL, ALUctr = "sub"
    
```

- nPC_sel <= if (OP == BEQ) then EQUAL
else 0
- ALUSrc <= if (OP == R-TYPE) then
"regB" else "immed"
- ALUctr <= if (OP == R-TYPE) then **funct**
elseif (OP == ORI) then "OR"
elseif (OP == BEQ) then "sub"
else "add"

- ExtOp <= if (OP == ORi) then "zero" else "sign"
- MemWr <= (OP == Store)
- MemtoReg <= (OP == Load)
- RegWr: <= if ((OP == Store) || (OP == BEQ)) then 0 else 1
- RegDst: <= if ((OP == Load) || (OP == ORi)) then 0 else 1

The diagram illustrates the internal components and data flow of the MIPS processor:

- Instruction Memory:** Receives `Instruction<31:0>` and provides register indices `Rs` (<21:25>), `Rt` (<16:20>), `Rd` (<11:15>), and an immediate value `Imm16` (<0:15>).
- PC (Program Counter):** Receives `nPC_sel` and `PC Ext` (from `imm16` via an adder). It outputs `PC` to a multiplexer and provides a `clk` signal.
- 32-bit Registers:** Contains registers `Rw`, `Ra`, and `Rb`. It receives `RegDst` (selecting between `Rd` and `Rt`) and `RegWr` (selecting between `Rw`, `Ra`, and `Rb`). It outputs `busA` and `busB` (32-bit).
- ALU (Arithmetic Logic Unit):** Receives `busA`, `busB`, and `ALUctr` (selecting between `add`, `MemWr`, and `MemtoReg`). It outputs a 32-bit result to the `ExtOp` multiplexer.
- ExtOp (Extender):** Takes the 32-bit ALU result and `imm16` (16-bit) as inputs. It selects between sign-extending the ALU result or zero-extending the `imm16` based on the `ExtOp` control signal.
- Data Memory:** Receives `WrEn` (write enable), `Adr` (address), and `Data In` (32-bit). It outputs data to the `MemtoReg` multiplexer.
- MemtoReg:** Selects between the ALU result and data from `Data Memory` based on the `MemtoReg` control signal.
- PC Mux:** Selects between the current `PC` and the next sequential PC (`PC + 4`) based on the `nPC_sel` control signal.

The diagram illustrates the logical vs. physical structure of a processor. It is divided into two main sections: **Control** and **Datapath**.

- Control Unit:**
 - Receives **Instruction** from **Ideal Instruction Memory**.
 - Sends **Control Signals** to the **Datapath**.
 - Receives **Conditions** from the **Datapath**.
- Datapath Unit:**
 - Instruction Address:** Receives the instruction address from the **PC** and outputs to **Ideal Instruction Memory**.
 - PC (Program Counter):** Receives the **Next Address** and outputs to the **Instruction Address**.
 - 32-bit Registers:**
 - Inputs: **Rd** (5 bits), **Rs** (5 bits), **Rt** (5 bits).
 - Outputs: **Rw** (32 bits), **Ra** (32 bits), **Rb** (32 bits).
 - Inputs: **Clk** (clock signal).
 - ALU (Arithmetic Logic Unit):**
 - Inputs: **A** (32 bits) and **B** (32 bits) from the registers.
 - Output: 32-bit result to the **Data Memory**.
 - Ideal Data Memory:**
 - Inputs: **Data Address** (32 bits) and **Data In** (32 bits).
 - Output: **Data Out** (32 bits).
 - Input: **Clk** (clock signal).

• Logical vs. Physical Structure

Summary

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic

Summary (cont.)

- MIPS makes it easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- Single cycle datapath => CPI=1, CCT => long
- Next time: implementing control