

---


# **Designs for Bipolar Logic Families**

**Somchai Prasitjutrakul**


---

# TTL : NAND Gates


---

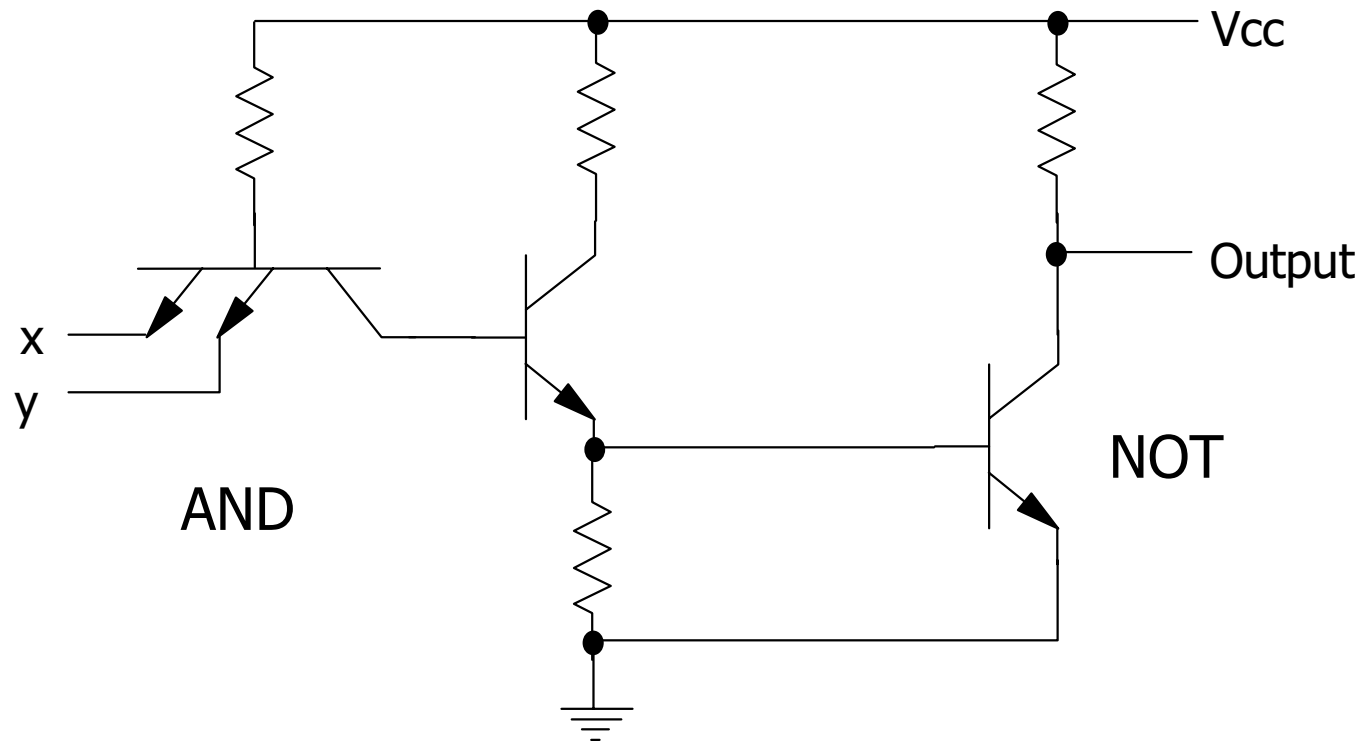


# TTL : NOR Gates

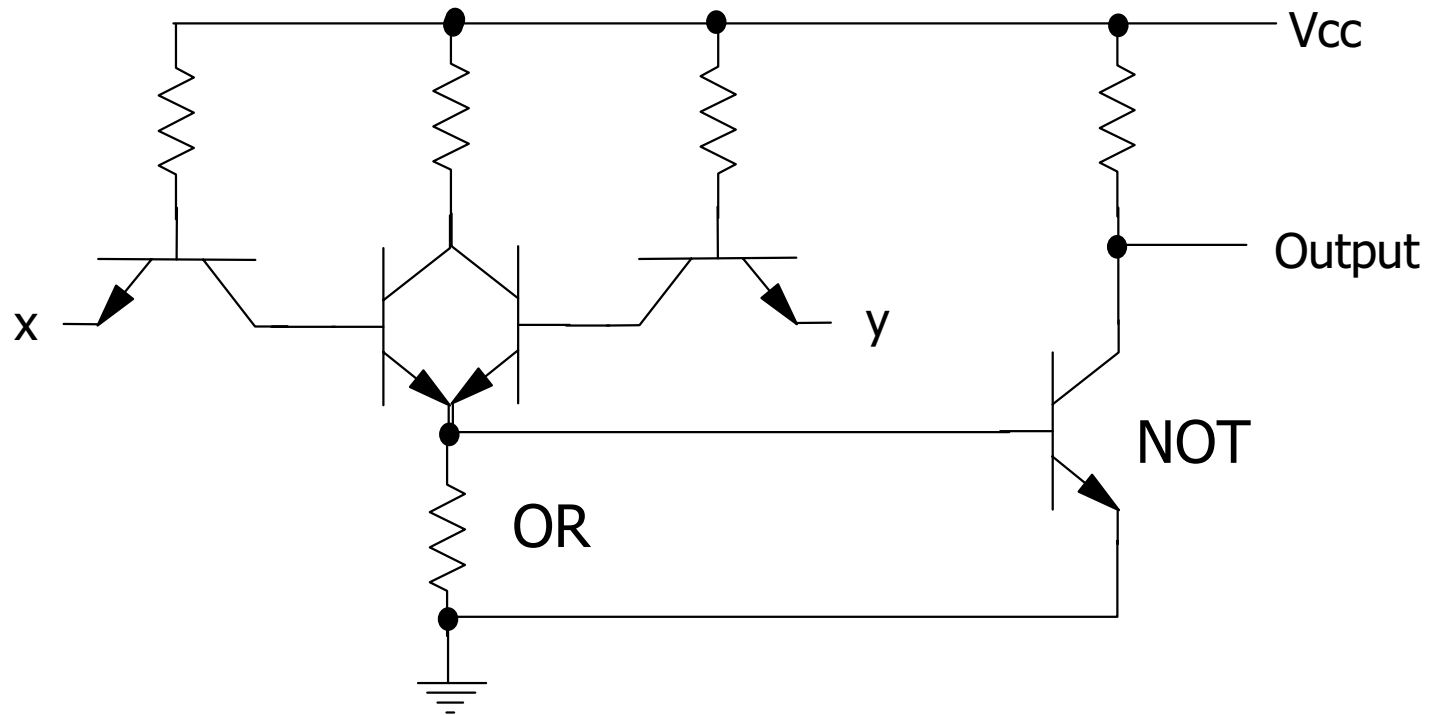



# TTL : AND-OR-INVERTER

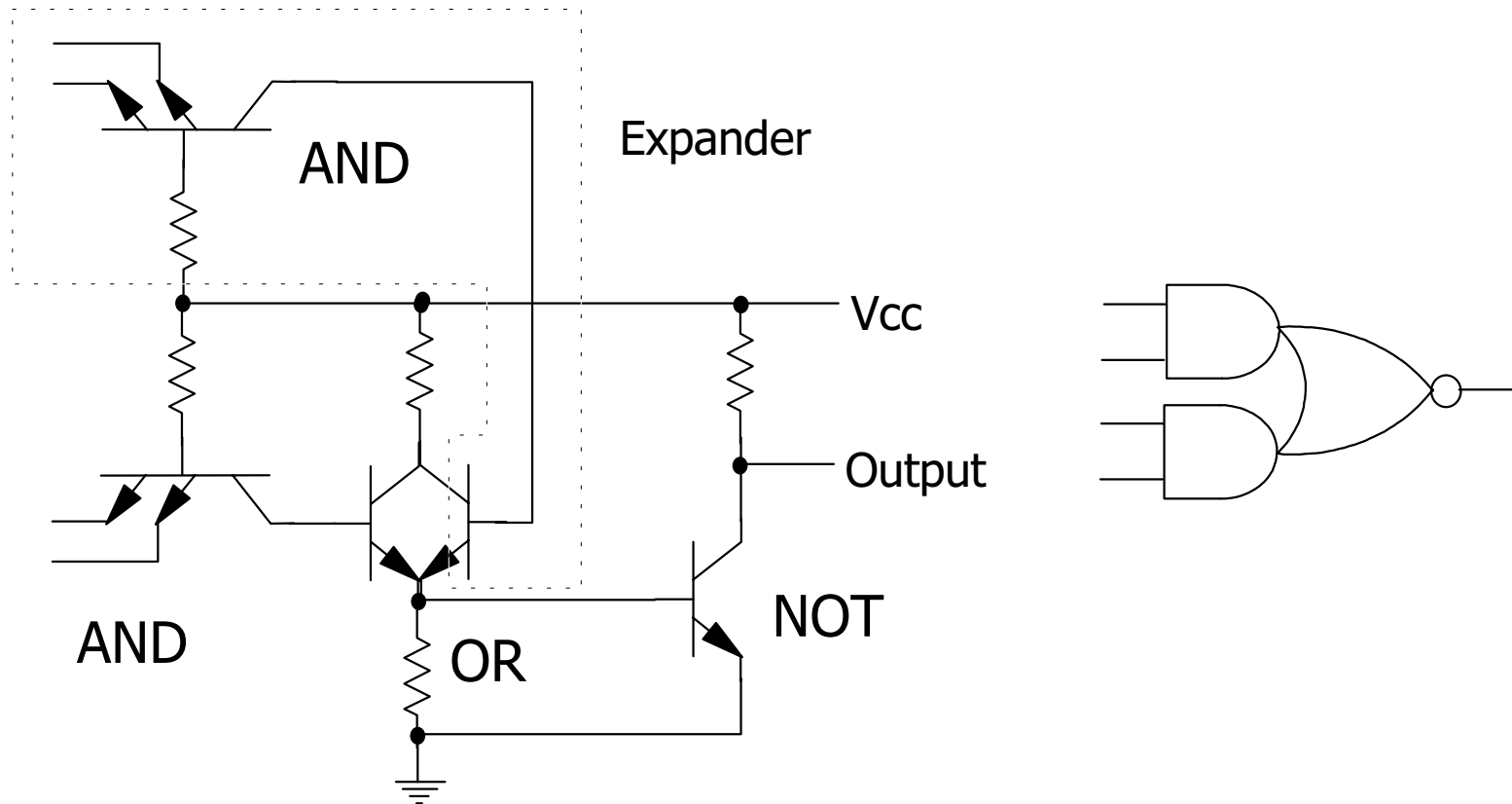


# TTL : AND Gates

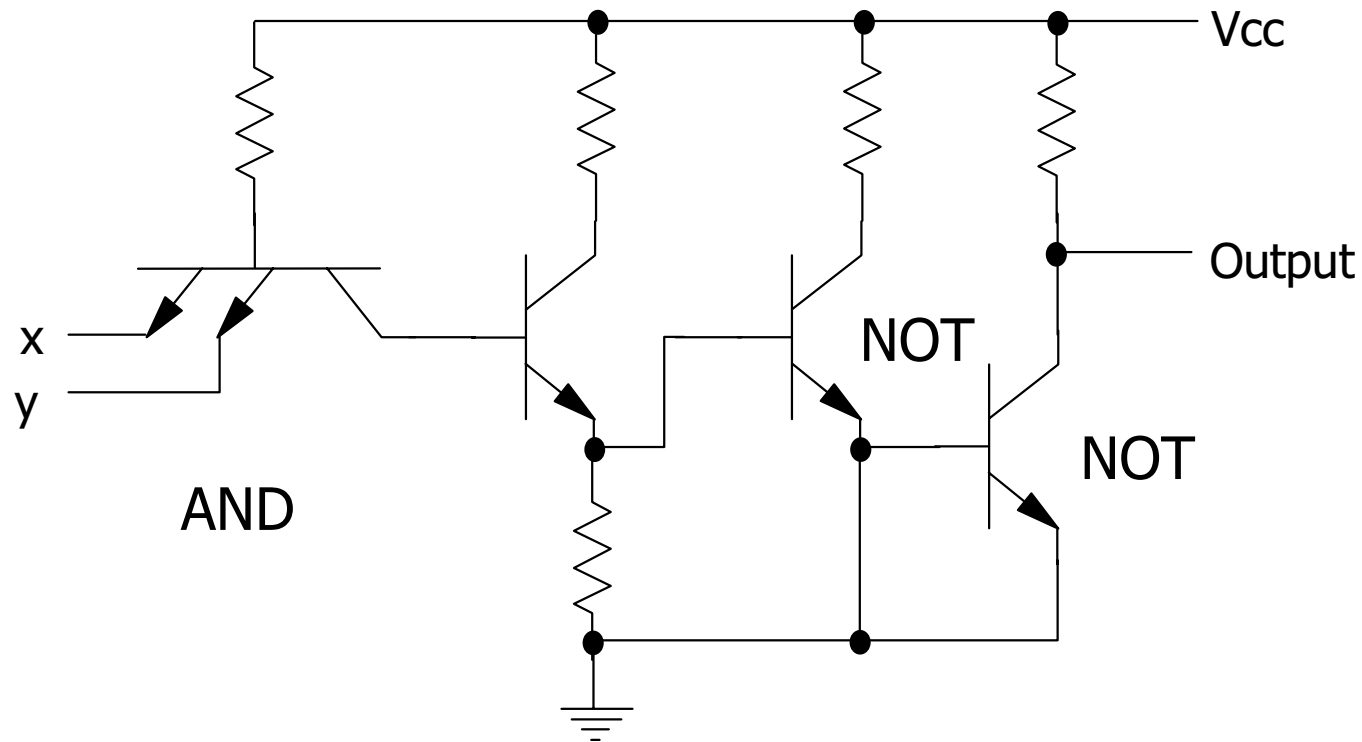


# Wired-AND of TTL Gates

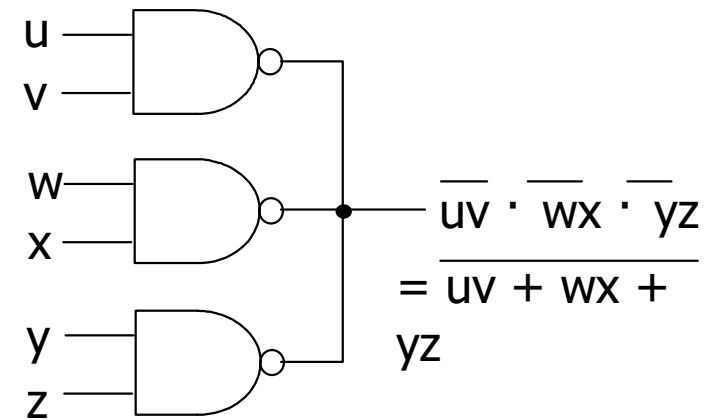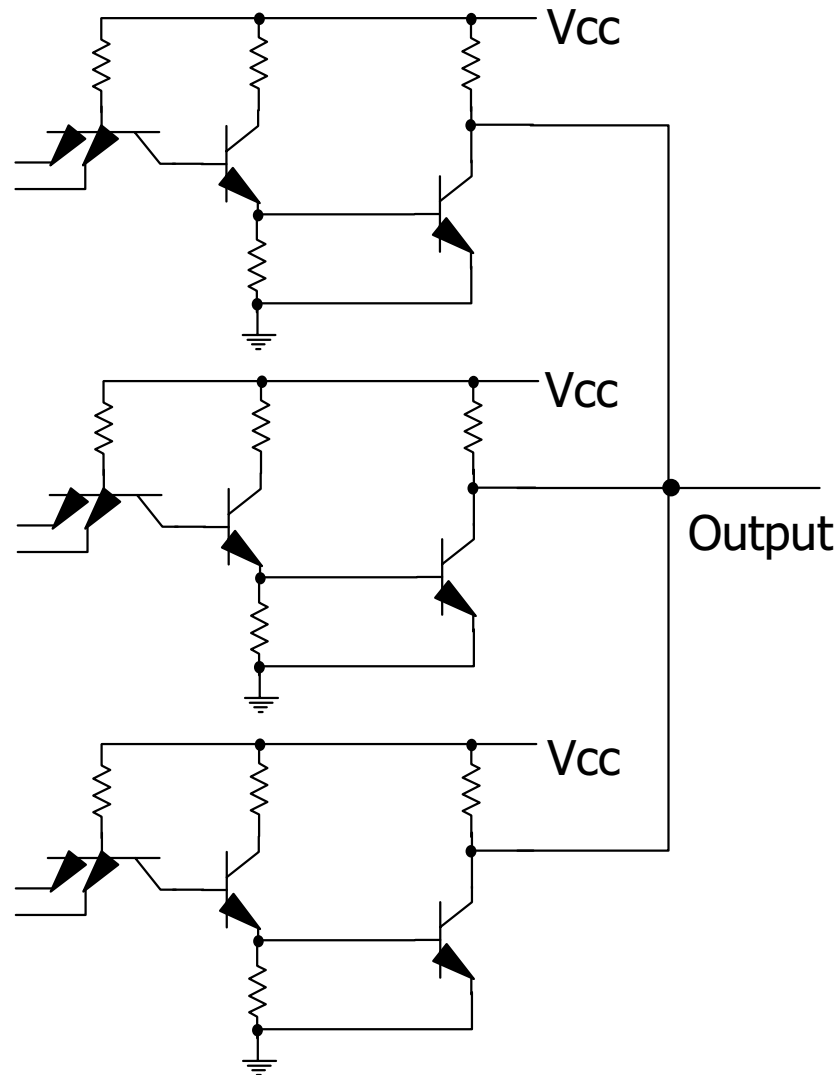

# Basic ECL Gates

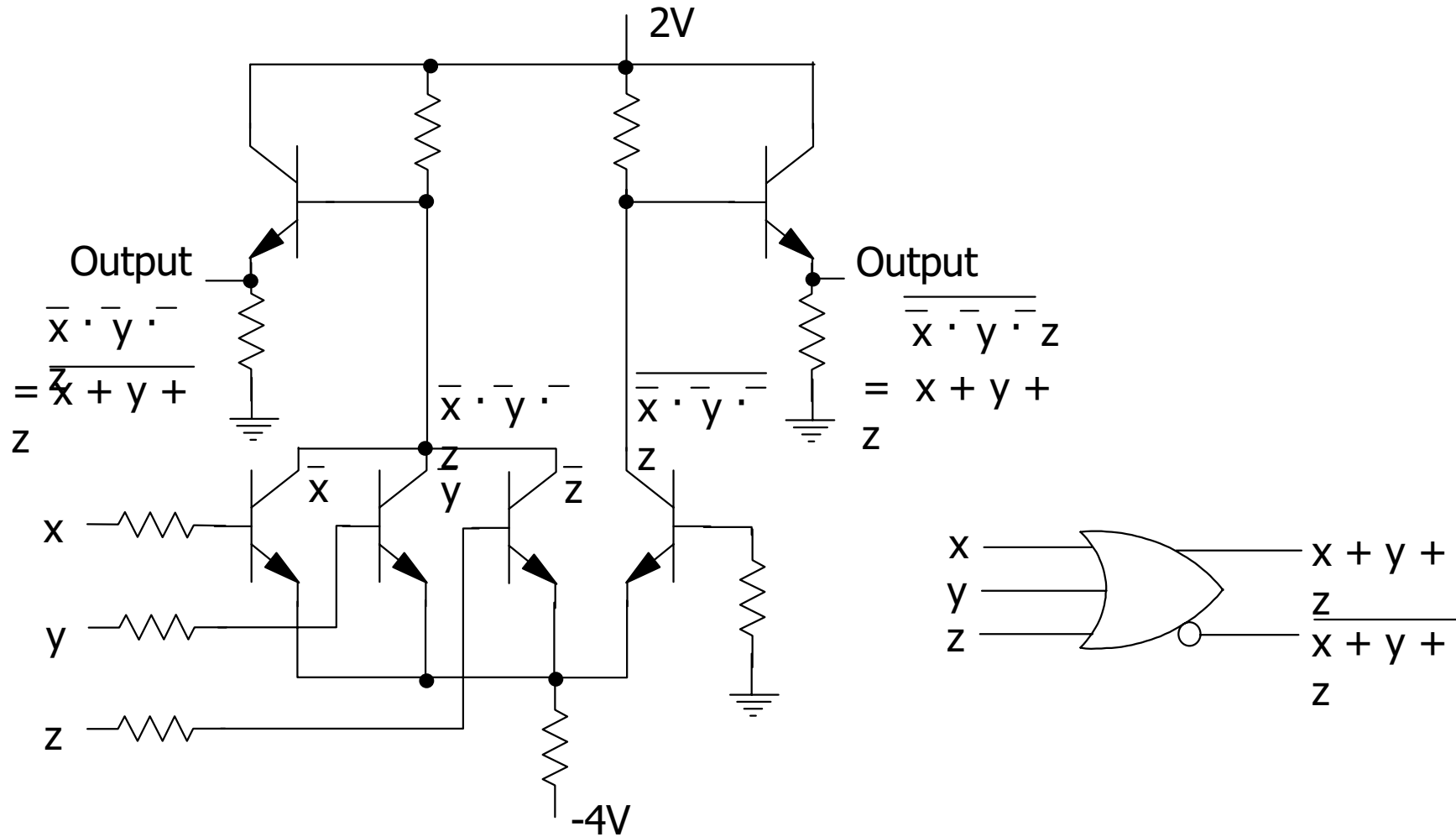


# Logic Operation of ECL gates

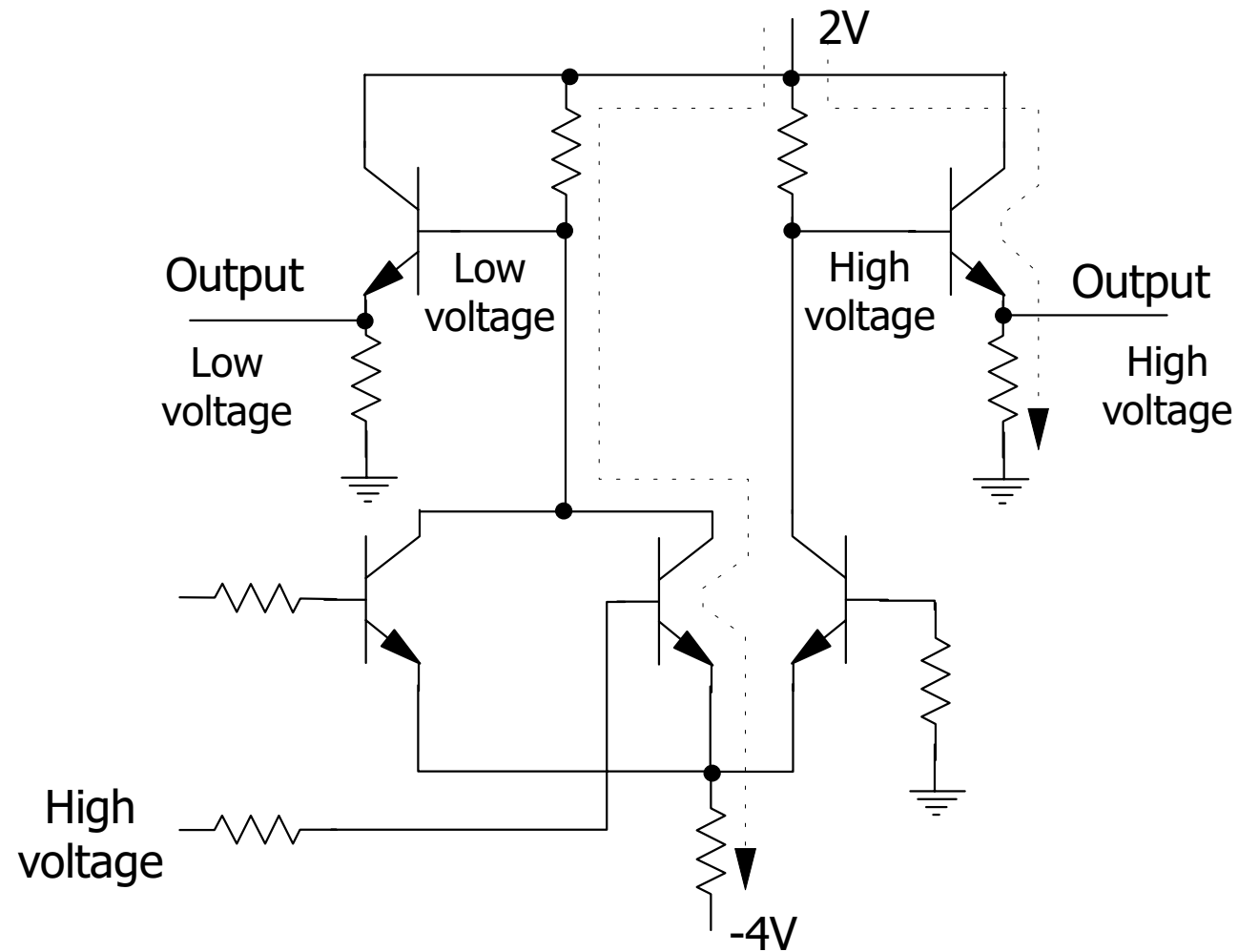




# Logic Operation of ECL gates

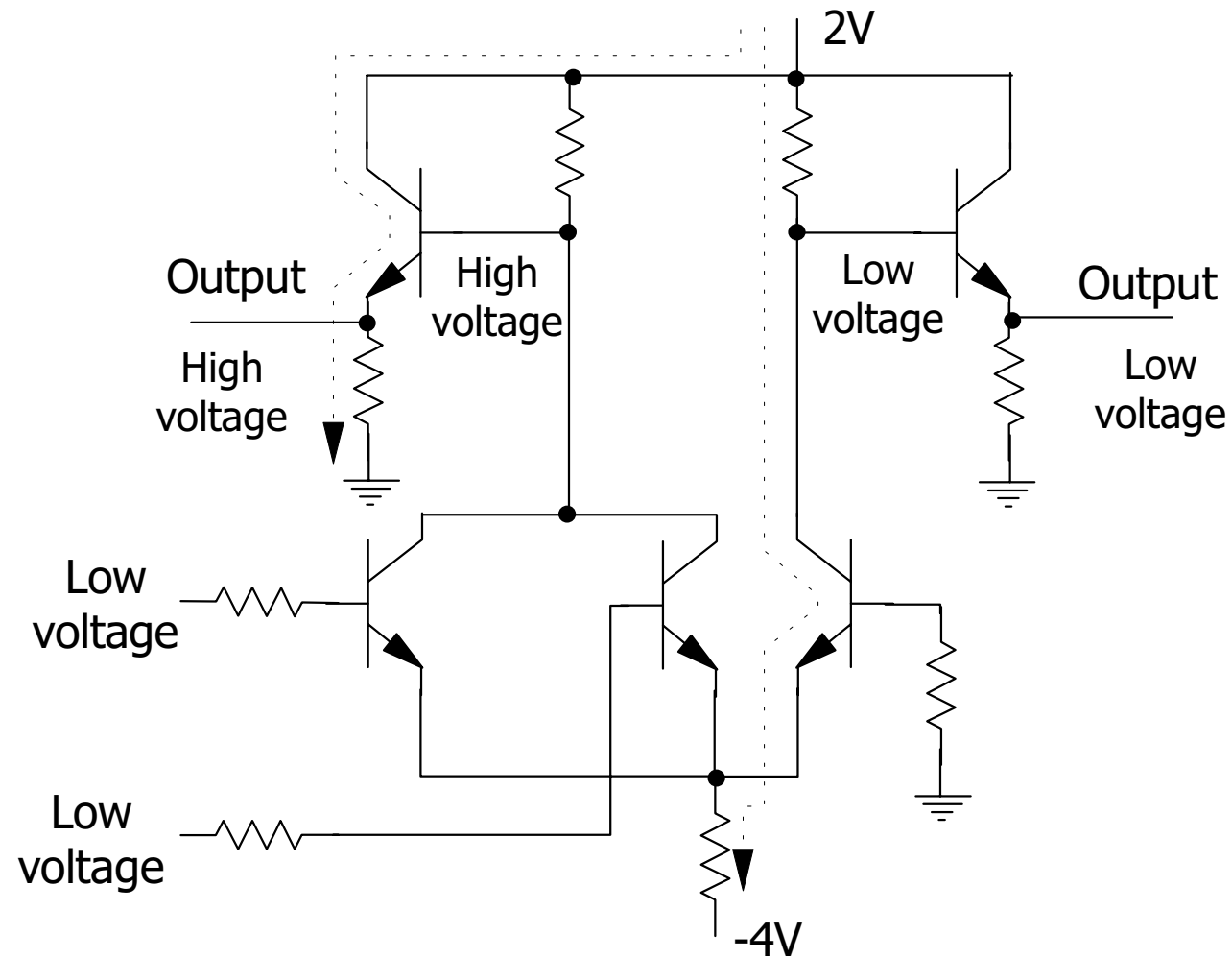


# Wired-OR of ECL Gates

---

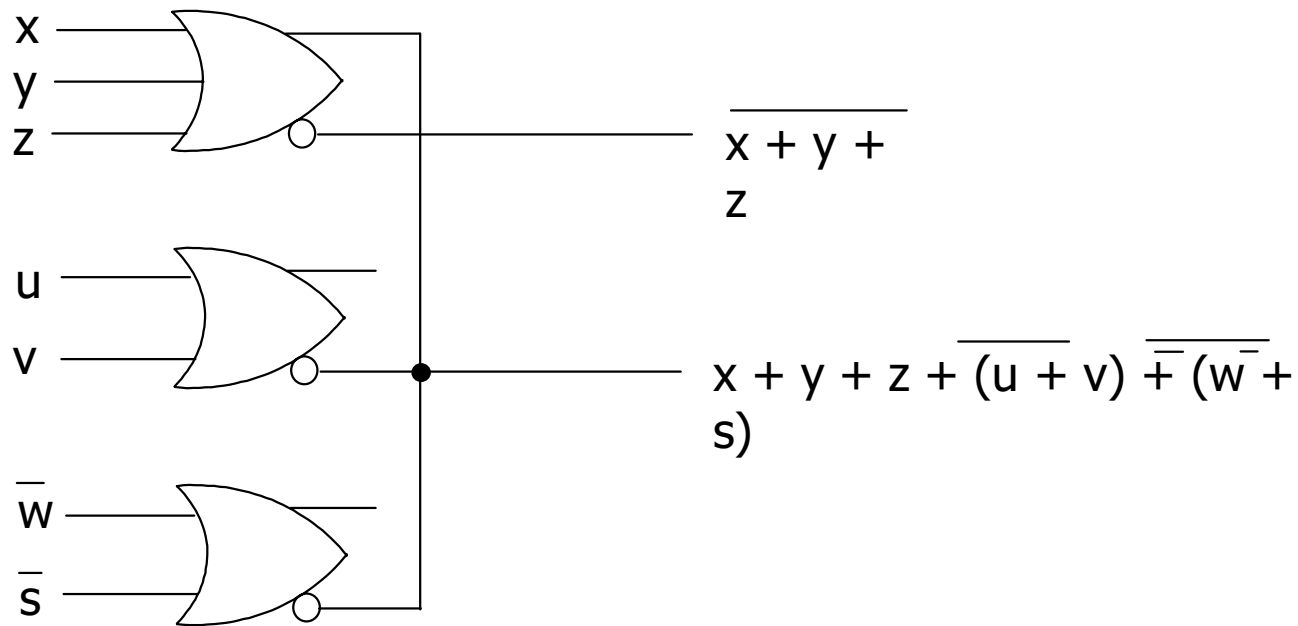

# Multiple-Output ECL gates

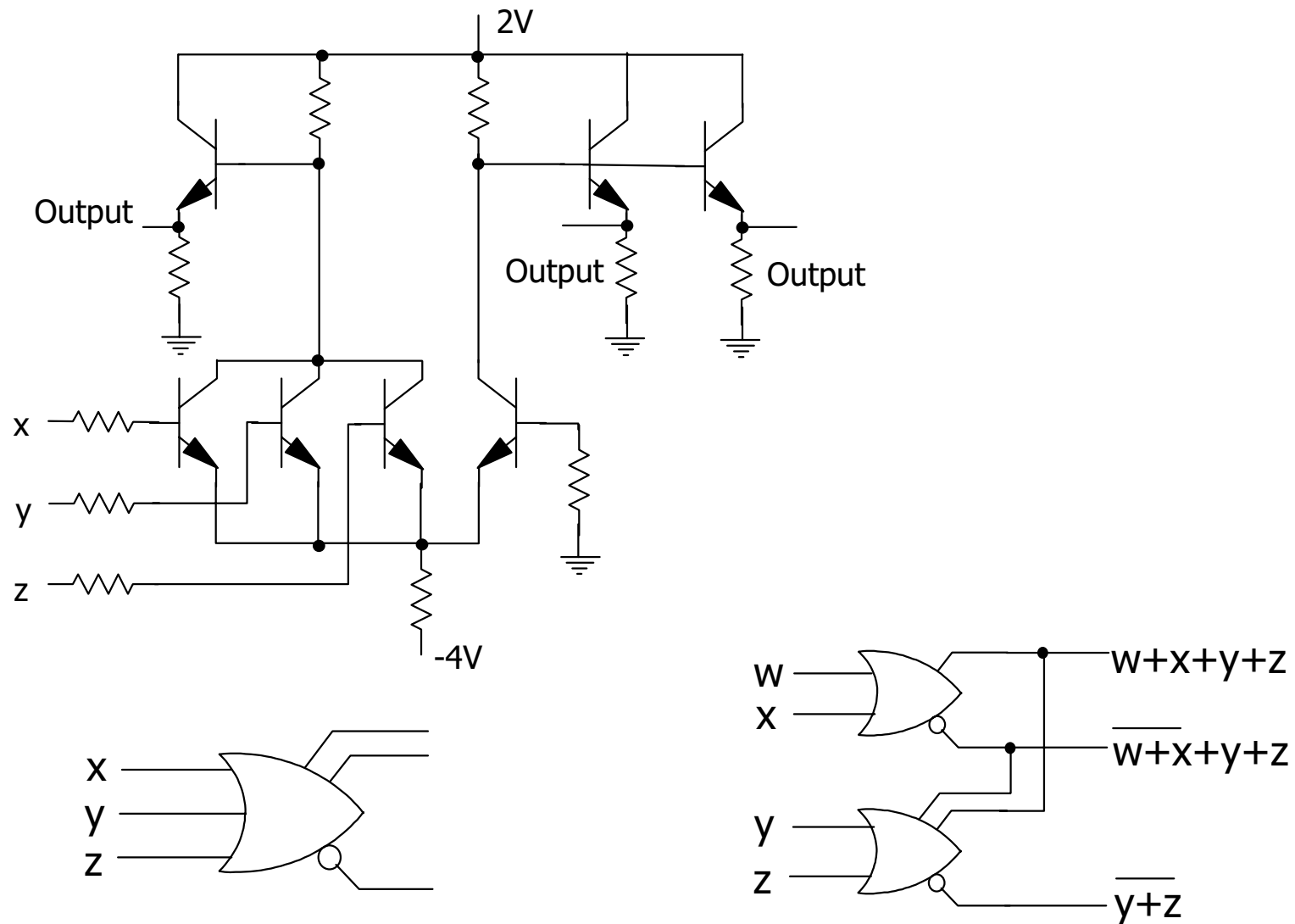

# Examples

